

HOMEWORK WEEK 4

17. **SSM WWW REASONING** The resistance of a metal wire of length L , cross-sectional area A and resistivity ρ is given by Equation 20.3: $R = \rho L / A$. The volume V_2 of the new wire will be the same as the original volume V_1 of the wire, where volume is the product of length and cross-sectional area. Thus, $V_1 = V_2$ or $A_1 L_1 = A_2 L_2$. Since the new wire is three times longer than the first wire, we can write

$$A_1 L_1 = A_2 L_2 = A_2 (3L_1) \quad \text{or} \quad A_2 = A_1 / 3$$

We can form the ratio of the resistances, use this expression for the area A_2 , and find the new resistance.

SOLUTION The resistance of the new wire is determined as follows:

$$\frac{R_2}{R_1} = \frac{\rho L_2 / A_2}{\rho L_1 / A_1} = \frac{L_2 A_1}{L_1 A_2} = \frac{(3L_1) A_1}{L_1 (A_1 / 3)} = 9$$

Solving for R_2 , we find that

$$R_2 = 9R_1 = 9(21.0 \, \Omega) = \boxed{189 \, \Omega}$$

21. **REASONING AND SOLUTION** According to Equation 20.6c, the power dissipated by the iron is

$$P = \frac{V^2}{R} = \frac{(120 \, \text{V})^2}{24 \, \Omega} = \boxed{6.0 \times 10^2 \, \text{W}}$$

23. **SSM REASONING** According to Equation 6.10b, the energy used is $\text{Energy} = Pt$, where P is the power and t is the time. According to Equation 20.6a, the power is $P = IV$, where I is the current and V is the voltage. Thus, $\text{Energy} = IVt$, and we apply this result first to the dryer and then to the computer.

SOLUTION The energy used by the dryer is

$$\text{Energy} = Pt = IVt = (16 \, \text{A})(240 \, \text{V})(45 \, \text{min}) \left(\frac{60 \, \text{s}}{1.00 \, \text{min}} \right) = 1.04 \times 10^7 \, \text{J}$$

Converts minutes
to seconds

For the computer, we have

$$\text{Energy} = 1.04 \times 10^7 \, \text{J} = IVt = (2.7 \, \text{A})(120 \, \text{V})t$$

Solving for t we find

$$t = \frac{1.04 \times 10^7 \text{ J}}{(2.7 \text{ A})(120 \text{ V})} = 3.21 \times 10^4 \text{ s} = (3.21 \times 10^4 \text{ s}) \left(\frac{1.00 \text{ h}}{3600 \text{ s}} \right) = \boxed{8.9 \text{ h}}$$

39. **SSM REASONING** Using Ohm's law (Equation 20.2) we can write an expression for the voltage across the original circuit as $V = I_0 R_0$. When the additional resistor R is inserted in series, assuming that the battery remains the same, the voltage across the new combination is given by $V = I(R + R_0)$. Since V is the same in both cases, we can write $I_0 R_0 = I(R + R_0)$. This expression can be solved for R_0 .

SOLUTION Solving for R_0 , we have

$$I_0 R_0 - IR_0 = IR \quad \text{or} \quad R_0(I_0 - I) = IR$$

Therefore, we find that

$$R_0 = \frac{IR}{I_0 - I} = \frac{(12.0 \text{ A})(8.00 \Omega)}{15.0 \text{ A} - 12.0 \text{ A}} = \boxed{32 \Omega}$$

41. **REASONING AND SOLUTION** The equivalent resistance of the circuit is

$$R_s = R_1 + R_2 = 36.0 \Omega + 18.0 \Omega = 54.0 \Omega$$

Ohm's law for the circuit gives $I = V/R_s = (15.0 \text{ V})/(54.0 \Omega) = 0.278 \text{ A}$

a. Ohm's law for R_1 gives $V_1 = (0.278 \text{ A})(36.0 \Omega) = \boxed{10.0 \text{ V}}$

b. Ohm's law for R_2 gives $V_2 = (0.278 \text{ A})(18.0 \Omega) = \boxed{5.00 \text{ V}}$

43. **SSM REASONING** The equivalent series resistance R_s is the sum of the resistances of the three resistors. The potential difference V can be determined from Ohm's law as $V = IR_s$.

SOLUTION

a. The equivalent resistance is

$$R_s = 25 \Omega + 45 \Omega + 75 \Omega = \boxed{145 \Omega}$$

b. The potential difference across the three resistors is

$$V = IR_s = (0.51 \text{ A})(145 \Omega) = \boxed{74 \text{ V}}$$